

Circuit theory:


Ohm's law $V = IR$

Theory

Kirchhoff's law: $\sum I_{in,i} = \sum I_{out,i} \Rightarrow \sum I_i = 0$

2: $\sum V_i = 0$ for a closed loop.

Potential divider:

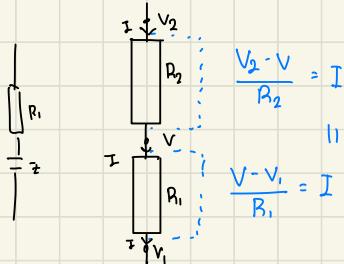

$$\frac{V_2 - V}{R_2} = I$$

$$\frac{V - V_1}{R_1} = I$$

$$\frac{V - V_1}{R_1} = \frac{V_2 - V}{R_2}$$

$$R_2(V - V_1) = R_1(V_2 - V)$$

$$R_2V - R_2V_1 = R_1V_2 - R_1V$$

$$R_1V + R_2V = R_1V_2 + R_2V_1$$

$$V(R_1 + R_2) = R_1V_2 + R_2V_1$$

$$V = \frac{R_1V_2 + R_2V_1 + V_1R_1 - V_2R_2}{(R_1 + R_2)}$$


$$V = \frac{R_1V_2 - V_1R_1 + V_1(R_1 + R_2)}{R_1 + R_2}$$

$$V = V_1 + \frac{(V_2 - V_1)R_1}{R_1 + R_2}$$

$$\text{if } V_1 = 0: V = \frac{V_2 R_1}{R_1 + R_2}$$

Complex numbers
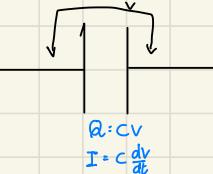
$$e^{i\theta} = \cos\theta + i\sin\theta$$



$$\cos(A+B) = \operatorname{Re}(e^{i(A+B)}) \quad \text{Cos wave is Re of } e^{i\theta}$$


$$= \operatorname{Re}(e^{iA} e^{iB}) \quad \text{Sin wave is Im of } e^{i\theta}$$

$$= \operatorname{Re}[(\cos A + i\sin A)(\cos B + i\sin B)]$$

$$= \cos A \cos B - \sin A \sin B$$

$$\text{Suppose } I = I_0 \sin \omega t \text{ ; } V = \frac{1}{C} \int I dt$$
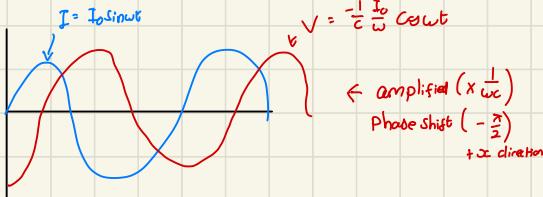
$$V = \frac{-1}{C} \frac{I_0}{\omega} \cos \omega t$$



$$\text{So } \tilde{V} = \tilde{I} \tilde{Z}$$


$$\text{Complex } \tilde{Z} \text{ arg. } = -\frac{\pi}{2} \Rightarrow \frac{1}{i\omega} \Rightarrow \tilde{Z} = \frac{1}{i\omega} e^{-i\frac{\pi}{2}} = \frac{1}{i\omega} = \tilde{Z}$$

$$Z = \frac{1}{i\omega C}$$


Same eq. as in AC.

Theory

Amplifiers:

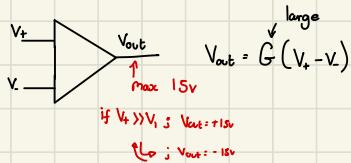

feedback:

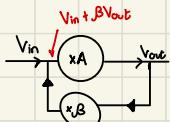

$$V_{out} = A(V_{in} + \beta V_{out})$$

$$V_{out} = A V_{in} + \beta A V_{out}$$

$$V_{out} = \frac{A V_{in}}{1 - \beta A}$$


$$\frac{V_{out}}{V_{in}} = \frac{A}{1 - \beta A} \quad A \rightarrow \infty \Rightarrow -\frac{1}{\beta} \quad \text{independent of } A$$

if A is large

Negative feedback ($\beta < 0$)

→ Stabilisation

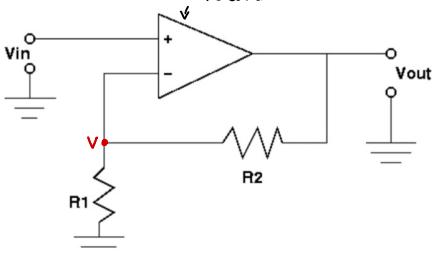$G \beta_1 \Rightarrow$ inputs draw no current




$$V = V_{out} \frac{R_1}{R_1 + R_2} = V_{in}$$

$G \beta_2 \Rightarrow$ in negative feedback circuits.

input voltages are adjusted to be equal.

$$V_{out} = G(V_{in} - V)$$

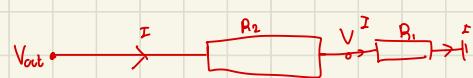

$$V = V_{out} \frac{R_1}{R_1 + R_2}$$

$$V_{out} = G(V_{in} - V_{out} \frac{R_1}{R_1 + R_2})$$

$$V_{out} = A(V_{in} + \beta V_{out})$$

$\beta = -\frac{R_1}{R_1 + R_2} \Rightarrow$ negative feedback
 • stable
 • doesn't depend on G

∴

$$\text{if } G \text{ is big: } \frac{V_{out}}{V_{in}} = -\frac{1}{\beta} = \frac{R_1 + R_2}{R_1}$$

Day 1:

Inverting Amplifier:

Theory:

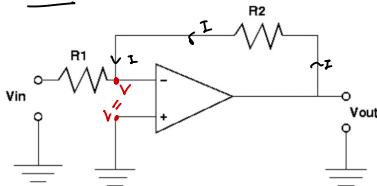


Figure 3. Inverting amplifier.

$$V_t = 0V \text{ (grounded)}$$

$$\text{as } V_i \approx V_- \text{ and } V_- = 0V \text{ (virtually grounded)}$$

$$\sum I_i = 0$$

$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{R_2}$$

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

Results:

At $(100 \pm 0.1) \text{ Hz}$

\downarrow

\downarrow

$R_1 / \text{k}\Omega$	Error	R_2	Error	Input PP / mV	Error / mV	Output PP / V	Error / V	Phase Shift / Degrees	Error Degrees
1	0.01	10	0.1	478	4	-4.78	0.04	179	1
1	0.01	100	5	105	2	-10.4	0.1	180	1

$$R_1 = 1 \text{ k}\Omega \text{ and } R_2 = 10 \text{ k}\Omega$$

$$\frac{V_{out}}{V_{in}} = -10$$

$$-\frac{R_2}{R_1} = -10$$

$$\sigma = 10 \times \sqrt{(0.01)^2 + (0.01)^2} \\ = 0.14$$

$$\sigma_{\text{ratio}} = \frac{V_{out}}{V_{in}} \sqrt{\left(\frac{4}{478}\right)^2 + \left(\frac{0.04}{478}\right)^2} \\ = 0.118$$

$$\frac{V_{out}}{V_{in}} = (10.0 \pm 0.1)$$

$$\text{Theory Suggests } \frac{V_{out}}{V_{in}} = -10 \pm 0.14$$

\Rightarrow Consistent

$$\text{Whereas in practice } \frac{V_{out}}{V_{in}} = -10.0 \pm 0.1$$

$$R_1 = 1 \text{ k}\Omega \text{ and } R_2 = 100 \text{ k}\Omega$$

$$\frac{V_{out}}{V_{in}} = 99.05$$

$$-\frac{R_2}{R_1} = -100$$

$$\sigma = 100 \times \sqrt{(0.05)^2 + (0.01)^2} \\ = 5.1$$

$$\sigma = \frac{V_{out}}{V_{in}} \sqrt{\left(\frac{2}{105}\right)^2 + \left(\frac{0.1}{104}\right)^2}$$

$$= 2.11$$

$$\frac{V_{out}}{V_{in}} = (99.05 \pm 2.11)$$

$$\text{Theory Suggests } \Rightarrow \frac{V_{out}}{V_{in}} = -100 \pm 5.1$$

\Rightarrow Consistent

$$\text{In practice } \Rightarrow \frac{V_{out}}{V_{in}} = (99.05 \pm 2.11)$$

V. was verified to be $\approx 0V$.

At high frequency: (100kHz): (using 1k Ω and 10k Ω)

$$V_{in} = (4.80 \pm 10)mV$$

$$\frac{V_{out}}{V_{in}} = -5.27 \pm 0.11 \quad (\text{using method as before})$$

$$V_{out} = (2.53 \pm 0.01)V$$

Expected is (10.0 ± 0.1) \therefore it can be seen that this relation breaks down at

high frequency \Rightarrow Gain is not infinite at high frequency

So approximation that $\frac{V_{out}}{V_{in}} = -\frac{1}{\beta}$ does not hold.

$$\text{Instead, } \frac{V_{out}}{V_{in}} = -\frac{G}{1+\beta G}$$

it can be seen from the data at low frequency that the phase shift is $\approx 180^\circ$ which is expected.

Summer

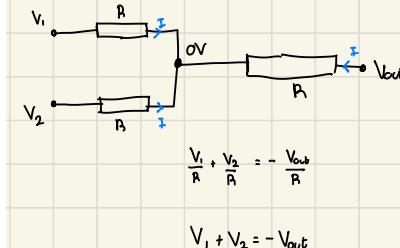
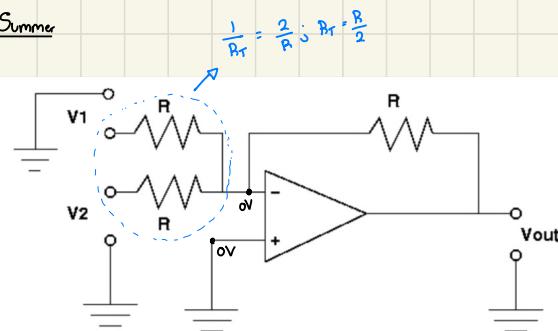


Figure 4. Summer.

R1 Kohm	Error Kohm	Input 1 mV	Error mV	Input 2 mV	Error mV	Output mV	Error mV	Phase / degrees	Error / degrees
10	0.1	454	4	510	10	960	10	179	1
1	0.01	434	4	490	10	920	10	181	1

for 10k Ω :

$$V_1 + V_2 = 9.64 \text{ mV}$$

$$\sigma = \sqrt{4^2 + 10^2} \text{ mV}$$

$$V_1 + V_2 = (9.64 \pm 11) \text{ mV}$$

$$V_{out} = (9.60 \pm 10) \text{ mV}$$

$$\text{Theory: } V_{out} = (9.64 \pm 11) \text{ mV}$$

$$\text{Experimentally: } V_{out} = (9.60 \pm 10) \text{ mV}$$

for 1k Ω :

$$V_1 + V_2 = 9.24$$

$$\sigma = \sqrt{4^2 + 10^2} \text{ mV}$$

$$V_1 + V_2 = (9.24 \pm 11) \text{ mV}$$

$$V_{out} = 9.20 \pm 10 \text{ mV}$$

$$\text{Theory: } V_{out} = (9.24 \pm 11) \text{ mV}$$

\Rightarrow Consistent for both R_f


$$\text{Experimentally: } V_{out} = (9.20 \pm 10) \text{ mV}$$

Also varied the phase difference between $V_1 + V_2$:

R1 Kohm	Error Kohm	Input 1 mV	Error mV	Input 2 mV	Error mV	Output mV	Error mV	Phase / degrees	Error / degrees
10	0.1	454	4	510	10	930	10	165	1
10	0.1	454	4	510	10	490	10	126	1
10	0.1	454	4	510	10	960	10	179	1

Summing law is only valid when waves have a phase difference of $n\pi$.

Integrator:

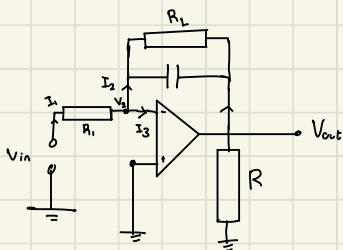

$$I = C \frac{dV}{dt}$$

$$V_{in} = V_0 \sin \omega t$$

$$R_L = 1 \text{ M}\Omega$$

$$f = (100 \pm 0.1) \text{ Hz}$$

$$I_3 \approx 0 \therefore I_1 = I_2$$

$$V_2 \approx 0 \quad \rightarrow \quad \frac{V_{in}}{R_1} = -C \frac{dV_{out}}{dt} \quad \text{Current through } R_L \approx 0$$

$$V_{out} = -\frac{1}{R_1 C} \int V_{in} dt$$

$$= -\frac{V_0}{R_1 C} \int \sin \omega t dt$$

$$V_{out} = \frac{V_0}{\omega R_1 C} \cos \omega t$$

$$\boxed{V_{out} = \frac{V_{in}}{\omega R_1 C}}$$

R1 kOhm	Error kOhm	C micro F	Error	Input mV	Error / mV	Output V	Error V	Phase Degrees	Error Degrees
1	0.01	0.1	5%	490	10	7.6	0.1	-90	1
1	0.01	0.1	5%	800	10	12.9	0.1	-90	1

$$V_{in} = 490 \text{ mV}$$

Theory

$$\frac{V_{in}}{R_1 C} = \frac{0.49}{200 \pi \times 10^{-9} \times 10^{-6}} = 7.80 \text{ V}$$

$$\sigma = \frac{V_{in}}{R_1 C} \sqrt{\left(\frac{0.01}{490}\right)^2 + \left(\frac{0.1}{100}\right)^2 + (0.01)^2 + (0.05)^2}$$

$$= 0.43 \text{ V}$$

$$V_{out} = (7.80 \pm 0.43) \text{ V}$$

Don't overlap
but close

Experimentally:

$$V_{out} = 7.6 \pm 0.1$$

$$V_{in} = 800 \text{ mV}$$

$$\frac{V_{in}}{R_1 C} = 12.73 \text{ V}$$


$$\sigma = 0.67$$

$$\text{Theory: } V_{out} = 12.73 \pm 0.67 \text{ V}$$

Consistent!,

$$\text{Experimentally: } V_{out} = 12.9 \pm 0.1 \text{ V}$$


Phase shifter:

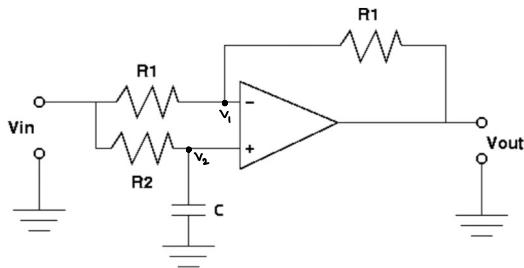

$$V = V_1 + (V_2 - V_1) \frac{R_1}{R_1 + R_2}$$

Figure 5. Phase shifter.

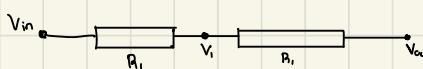
$$Z = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$



$$V_1 = V_{out} + (V_{in} - V_{out}) \frac{R_1}{2R_1}$$

$$V_1 = \frac{1}{2} (V_{in} + V_{out})$$

Equal for negative feedback

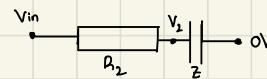

$$V_2 = -V_{in} \frac{\frac{1}{j\omega C}}{R_2 - \frac{1}{j\omega C}}$$

$$(V_{in} + V_{out}) = 2V_{in} \left[\frac{\frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} \right]$$

$$V_{out} = 2V_{in} \left[\frac{\frac{1}{j\omega C}}{\frac{1}{R_2 + \frac{1}{j\omega C}}} - \frac{1}{2} \right]$$

$$= 2V_{in} \left[\frac{1}{R_2 \omega C j + 1} \times \frac{1 - R_2 \omega C j}{1 + R_2 \omega C j} - \frac{1}{2} \right]$$

$$= 2V_{in} \left[\frac{1 - R_2 \omega C j}{1 + (R_2 \omega C)^2} - \frac{1}{2} \right]$$

looking for $V_{out} = \infty V_{in}$
complex

$$\infty = \frac{2 - 2R_2 \omega C j - 1 - (R_2 \omega C)^2}{1 + (R_2 \omega C)^2}$$

$$\infty = \frac{1 - (R_2 \omega C)^2 - 2R_2 \omega C j}{1 + (R_2 \omega C)^2}$$

$$\arg \infty = \arctan \left(\frac{2R_2 \omega C}{1 - (R_2 \omega C)^2} \right) = 60^\circ$$

$$\frac{R_2 \omega C}{1 - (R_2 \omega C)^2} = \frac{\sqrt{3}}{2}$$

$$-\frac{\sqrt{3}}{2} + \frac{\sqrt{3}}{2} R_2^2 \omega^2 C^2 + R_2 \omega C = 0$$

quadratic eqn in R_2

if $\omega = 2000\pi$, $C = 10\text{ nF}$

$$R_2 = 9188.8 \Omega$$

∴ phase difference of 60° is achieved roughly by $R = 10\text{ k}\Omega$ and $C = 10\text{ nF}$ at $f = 1000\text{ Hz}$

Gain Limitation:

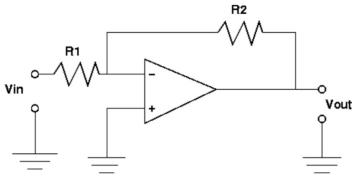


Figure 3. Inverting amplifier.

$$R_1 = 1 \text{ k}\Omega \quad R_2 = 10 \text{ k}\Omega / 100 \text{ k}\Omega$$

Check 1:

μ Fall/ns	Error on Fall/ μ ns	Pk-Pk/mV	Error on Pk-Pk/mV	Frequency/kHz	R1/kOhms	Error on R1/kOhms	R2/kOhms	Error on R2/kOhms
3.9	0.1	190	5	100	1	0.01	100	5
Fall/ns	Error on Fall/ns	Pk-Pk/mV	Error on Pk-Pk/mV	Frequency/MHz	R1/kOhms	Error on R1/kOhms	R2/kOhms	Error on R2/kOhms
300	10	140	5	1.2	1	0.01	10	0.1

$$\text{for the } 10 \text{ k}\Omega : \quad P_h - P_L = (140 \pm 5) \text{ mV}$$

$$\text{Fall time} = (300 \pm 10) \text{ ns}$$

$$\sigma = 4.6 \times 10^5 \times \sqrt{\left(\frac{10}{300}\right)^2 + \left(\frac{5}{140}\right)^2}$$


$$\text{Slew rate} = \frac{140 \times 10^3}{300 \times 10^{-9}} = (4.6 \pm 0.22) \times 10^5 \text{ Vs}^{-1} = 2.2 \times 10^4$$

$$\text{For } 100 \text{ k}\Omega : \quad P_h - P_L = 140 \pm 5 \text{ mV}$$

$$\text{fall time} = 3.9 \mu\text{s} \pm 0.1 \mu\text{s}$$

$$\text{Slew rate} = \frac{140}{3.9 \times 10^3} = (3.67 \pm 0.18) \times 10^4 \text{ Vs}^{-1} \quad \sigma = 4.6717 \sqrt{\left(\frac{5}{140}\right)^2 + \left(\frac{0.1}{3.9}\right)^2} \approx 1781 \text{ Vs}^{-1}$$

Check 2+3:

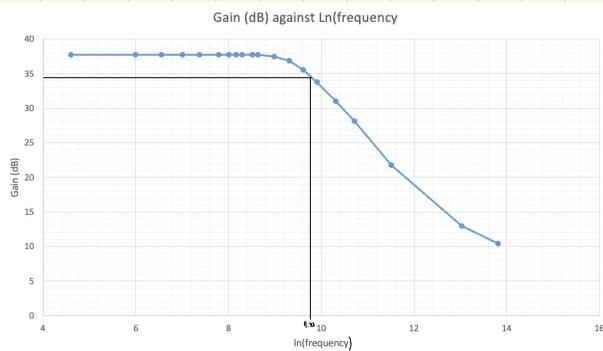

↳ graph for the $100 \text{ k}\Omega$ register

-3dB point, gain is $\frac{1}{\sqrt{2}}$ of original
 $\frac{1}{\sqrt{2}} (38) = 54.6$


↳ in dB $\rightarrow 34.74$

$$\ln(f) \approx 9.75$$

$$f = e^{\frac{9.75}{2}} = 17150 \text{ Hz} \Rightarrow -3 \text{dB point for } 100 \text{ k}\Omega$$

inverting amplifier circuit

and for the 10k₂ resistor:

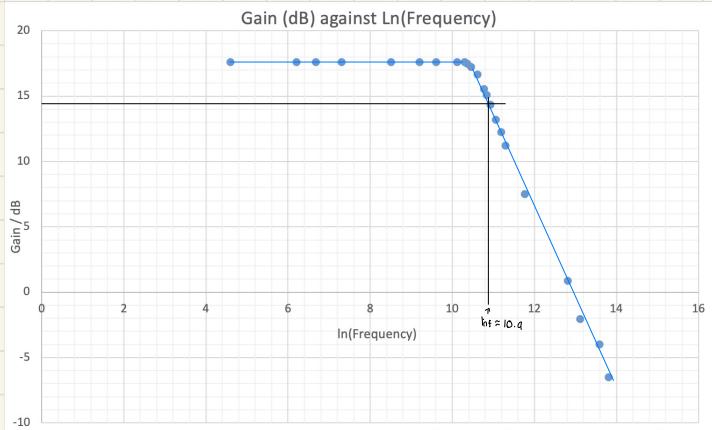

$$\text{Max gain} = 7.56$$

$$\frac{1}{\sqrt{2}} (7.56) = 5.35$$

$$\text{in dB} = 14.56 \text{ dB}$$

$$\ln f \approx 10.2$$




$$f \approx 54175 \text{ Hz}$$

It can be seen that bandwidth increases as gain decreases.

Check 4: at 1 MHz $\Rightarrow \varphi = -45^\circ \pm 2$

at 370 Hz $\Rightarrow \varphi = 180^\circ \pm 1$

Output impedance:

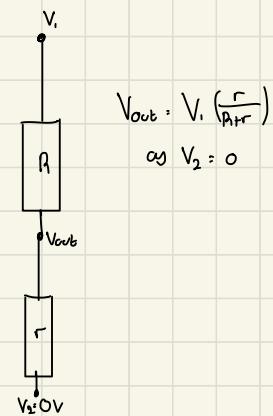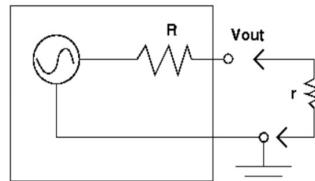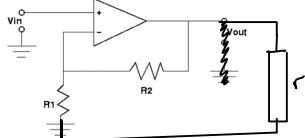

Check 1:

High frequency used so gain was not infinite. Used 1 MHz

Connected a small resistance resistor in parallel with the output terminal.

Peak - Peak output voltage with no resistor = $V_1 = 0.31 \pm 0.01 \text{ V}$

With resistor $\Rightarrow V_2 = 0.23 \pm 0.01 \text{ V}$

Voltage drop:

$$\frac{V_2}{V_1} = \frac{r}{(R+r)}$$

$$R = \frac{V_1 V_2}{V_2 - V_1} - r$$

$$= \frac{100 \times 0.31}{0.23} - 100 = 34.78 \Omega$$

$$\sigma = \frac{r V_1}{V_2} \sqrt{\left(\frac{0.01}{0.31}\right)^2 + \left(\frac{0.01}{0.23}\right)^2 + \left(\frac{0.01}{0.23}\right)^2}$$

$$= 7.42$$

$$\sigma_R = \sqrt{(7.42)^2 + 1^2} = 7.49 \Omega$$

Using $r = 100 \Omega \pm 1 \Omega$

$$So R = (34.78 \pm 7.49) \Omega \leftarrow \text{internal resistance.}$$

This cannot be measured with $r = 10k\Omega$ as this is much larger than R :

$$\frac{V_2}{V_1} = \frac{r}{R_1 + r} \Rightarrow \text{denominator would be } \approx r$$



So R cannot be determined.

$$\therefore \frac{V_2}{V_1} \approx 1, \text{ no difference in voltage measurements.}$$


Day 2:

$$V_f \neq V \Rightarrow \text{positive feedback.}$$

Schmitt trigger

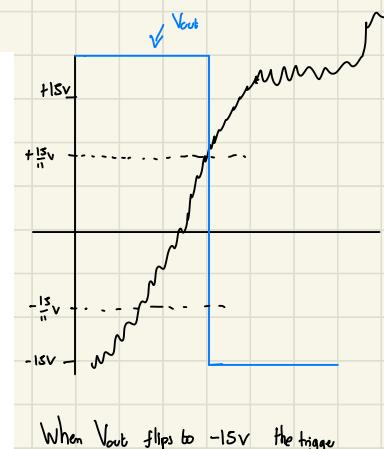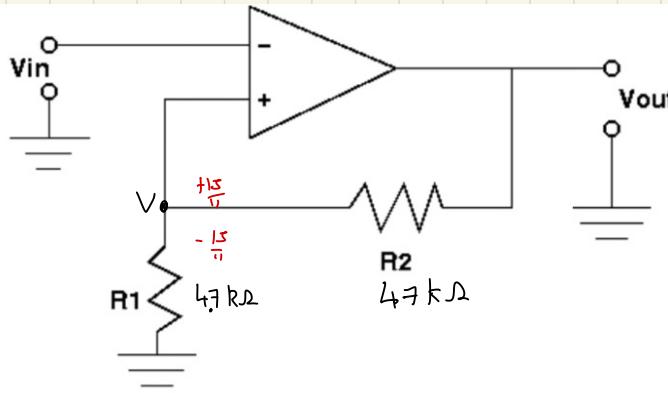

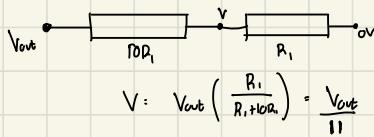When V_{out} flips to $-15V$ the trigger point also flips to $-\frac{15}{11}V$ so noise won't flip V_{out} .



$$V = V_{out} \left(\frac{R_1}{R_1 + R_2} \right) = \frac{V_{out}}{11}$$

Point at which output flips from $+15V$ to $-15V$

$$\text{Should be } V_f = \frac{R_1}{R_1 + R_2} V_{out}$$

$$= \frac{4.7}{4.7 + 10} 15 = \frac{15}{11} V = 1.36V$$

$$R_1 = 4.7 k\Omega \pm 0.047 k\Omega$$

$$R_2 = 4.7 k\Omega \pm 2.35 k\Omega$$

Measured to be: $V_f = 1.29 \pm 0.02V$, $V_f = -1.33 \pm 0.02V$

This difference is due to the output voltage is

Not equal to $15V$ experimentally it is $13.8 \pm 0.02V$

In theory: $V_r = \frac{13.81}{11} = 1.26 \pm 0.06 \text{ V}$

$$\sigma_{V_r} = 1.25 \sqrt{\left(\frac{0.02}{13.81}\right)^2 + \left(\frac{0.0042}{0.09}\right)^2} = 0.06$$



$$V_- = \frac{-13.75}{11} = -1.25 \pm 0.06 \text{ V}$$

So $V_r = 1.29 \pm 0.02 \text{ V}$ (measured) is consistent with theory $\rightarrow V_r = 1.26 \pm 0.06 \text{ V}$

$V_- = -1.33 \pm 0.02 \text{ V}$ (measured) is consistent with theory $\rightarrow V_- = -1.25 \pm 0.06 \text{ V}$

$$\begin{aligned} R_1 + R_2 &= 51.7 \pm 2.35 \text{ k}\Omega \\ \sigma &= \sqrt{(0.047)^2 + (2.35)^2} = 2.35 \\ \frac{R_1}{R_1 + R_2} &= \frac{1}{11} = 0.09 \pm 0.0042 \\ \sigma &= \frac{1}{11} \sqrt{(0.01)^2 + \left(\frac{2.35}{0.09}\right)^2} = 0.0042 \end{aligned}$$

Astable multivibrator:

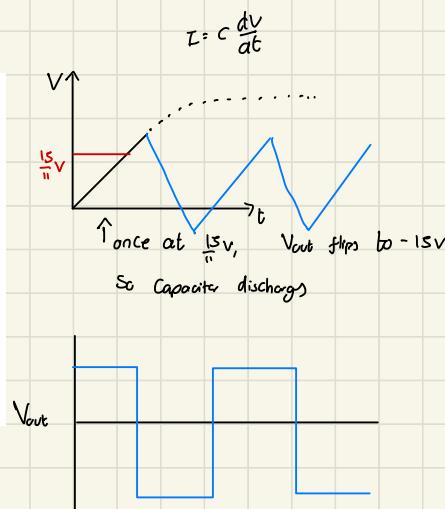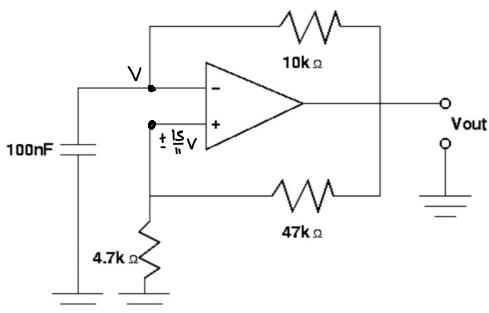

Output is square wave. And set input frequency = output

$$I = C \frac{\Delta V}{\Delta t} \Rightarrow \text{finite region}$$

$$\Delta t = \frac{C}{I} \Delta V$$

$$f = \frac{I}{C} \frac{1}{\Delta V}$$

$$\Delta V: 5.03V \pm 0.02V \leftarrow \text{measured}$$

$$I = \frac{V}{R} = \frac{13.56 - 2.5}{10 \times 10^3} = 1.106 \text{ mA} \Rightarrow \text{Current through } 10 \text{ k}\Omega \text{ resistor}$$

$$\sigma_V = \sqrt{\left(\frac{0.02}{13.56}\right)^2 + \left(\frac{0.02}{2.5}\right)^2} \approx 8.13 \times 10^{-3}$$

$$V_{\text{out}}: (13.56 \pm 0.02) \text{ V}$$

$$\sigma_I = I \sqrt{\left(\frac{8.13 \times 10^{-3}}{1.106}\right)^2 + (0.01)^2} \approx 0.011 \text{ mA}$$

$$f = \frac{1.106 \times 10^{-3}}{100 \times 10^{-9}} \frac{1}{5.03} = 2198.8 \text{ Hz}$$

$$\sigma_f = f \sqrt{\left(\frac{0.011}{1.106}\right)^2 + (0.05)^2 + \left(\frac{0.02}{5.03}\right)^2}$$

$$\sigma_f = 112.4 \text{ Hz}$$



$$f = 2198 \pm 0.112 \text{ kHz} \leftarrow \text{theory}$$

Consistent with measured value

$$\text{Measured } f = 2142 \pm 0.001 \text{ kHz}$$

Wien Bridge oscillator

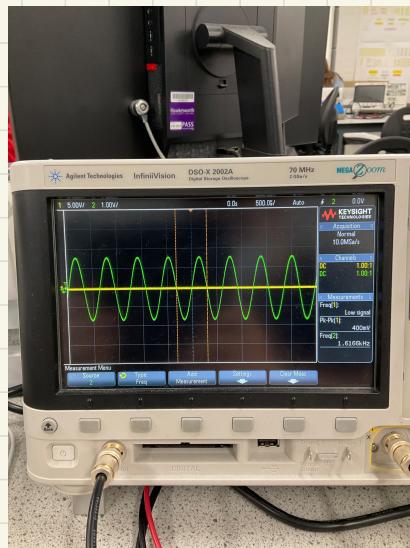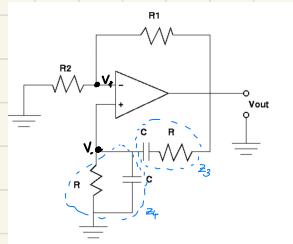$f_{\text{out}} = 1.61 \pm 0.01 \text{ kHz} \rightarrow \text{Error as 0.01 oscillation on reading.}$



We used the oscilloscope to measure the maximum

peak to peak V_i to be $1.6 \pm 0.1 \text{ V}$

by connecting

and V_i to be $1.6 \pm 0.1 \text{ V}$.

One end to ground

They are they are the same.

and one to the measured

point.

↓
negative feedback

$$\frac{R_1}{R_2} = \frac{Z_3}{Z_4} = \frac{1}{Z_1} Z_3$$

$$Z = \frac{1}{i\omega C}$$

$$Z_3 = \frac{1}{j\omega C} + R$$

$$\frac{1}{Z_4} = j\omega C + \frac{1}{R}$$

$$\frac{Z_3}{Z_4} = \left(j\omega C + \frac{1}{R}\right) \left(\frac{1}{j\omega C} + R\right)$$

$$= 1 + j\omega RC + \frac{1}{j\omega RC} + 1$$

$$= 2 + \frac{1}{j\omega RC} + j\omega RC$$

$$\frac{R_1}{R_2} = 2 + \left(\omega RC - \frac{1}{\omega RC}\right) j$$

$$R\omega C = \frac{1}{\omega RC}$$

$$R^2 \omega^2 C^2 = 1$$

$$\omega = \frac{1}{RC}$$

$$f = \frac{1}{2\pi RC}$$

$$\text{Now: } R = 10^4 \pm 1\% \Omega$$

$$= 10^4 \pm 10^2 \Omega$$

$$C = 10^{-8} \pm 20\% \text{ F}$$

$$\text{So } f = \frac{1}{2\pi RC} = 1592 \text{ Hz}$$

$$\sigma_f = f \sqrt{(0.01)^2 + (0.2)^2}$$

$$= 319 \text{ Hz}$$

$$\text{So } f = 1590 \pm 320 \text{ Hz}$$

$$f = 1.59 \pm 0.32 \text{ kHz}$$

← Theoretical

Measured $f = 1.61 \pm 0.01 \text{ kHz}$


↗ Consistent

No complex term in $\frac{R_1}{R_2}$


Flash ADC:

Dc33

Now using LM311 chip instead of 741 chip

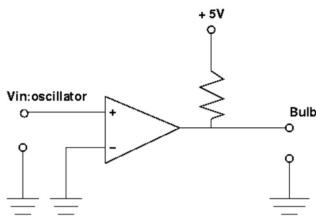


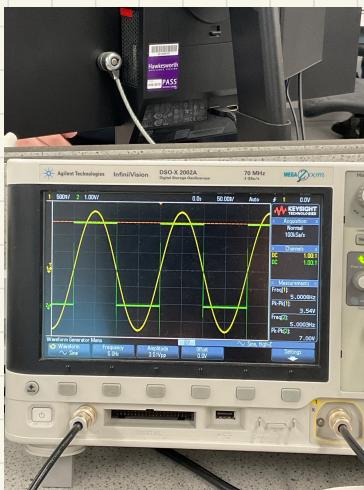Using a frequency of 5 MHz allowed us to see the LED flashing confirming Comparator works.
Then changing this output to display on the oscilloscope gave a digital output further confirming the comparator works.



- Then using the filament bulb the bulb did not light up. This is due to a low current.
- With the bulb, the square wave output had a smaller amplitude.

2-bit ADC:

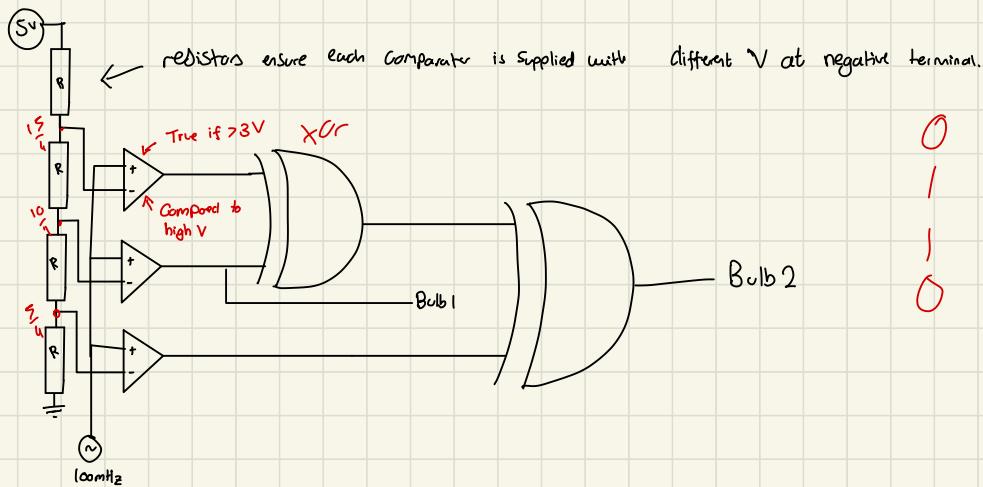



With this circuit, neither bulb will light for $V_{in} \leq 1V$

Bulb 2 will light for $1V < V_{in} \leq 2V$

Bulb 3 will light for $2V < V_{in} \leq 3V$

both will light for $V_{in} > 3V$


Schmitt trigger

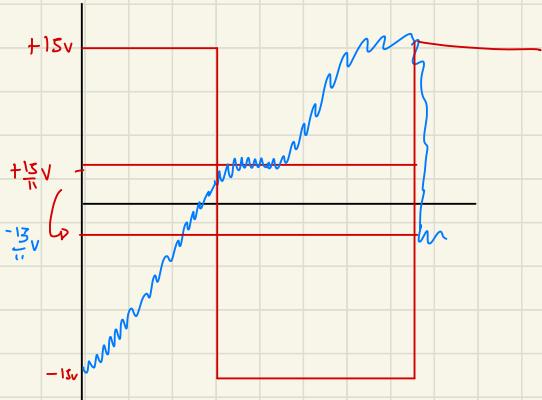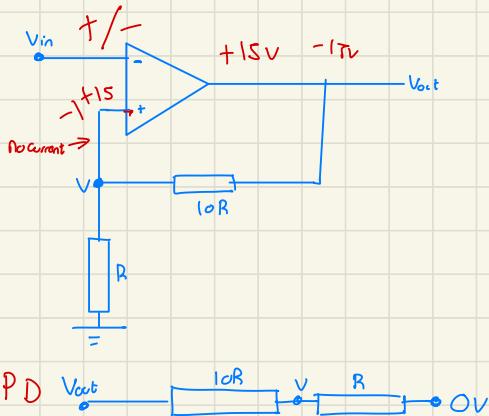

$$V = V_{out} \frac{R}{10R} = \frac{V_{out}}{10}$$

$$V = \frac{1}{10} V_{out}$$

Normal Comparator:

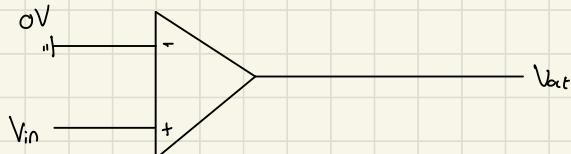

when $V_{in} < 0$, $V_{out} = -15V$

$V_{in} > 0$ $V_{out} = +15V$

